


# Computer Studies

bijan.veyssi-galmiche

March 2020
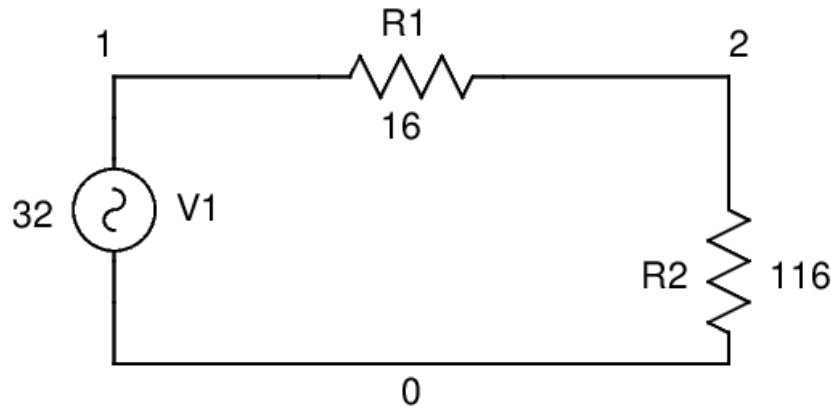
## 1 Gschem

I learnt to use gschem, it was pretty easy since it is very intuitive. You will find what I did on it beneath.



*Here is the scheme obtained after printing*

## 2 Ngspice

```
* Spice netlister for gnetlist
R2 0 2 116
R1 1 2 16
V1 1 0 32
.END
```

*Here is .net file obtained*

### 3 Results

```
ngspice 1 -> source 01.net
```

```
Circuit: * spice netlister for gnetlist
```

```
ngspice 1 -> tran 5 1
```

```
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
```

```
Initial Transient Solution
```

```
-----
```


Node	Voltage
----	-----
2	28.1212
1	32
v1#branch	-0.242424

```
No. of Data Rows : 59
```

```
ngspice 1 -> plot "1"
```

```
ngspice 1 -> plot "2"
```

**Here is the result of plot "1"**

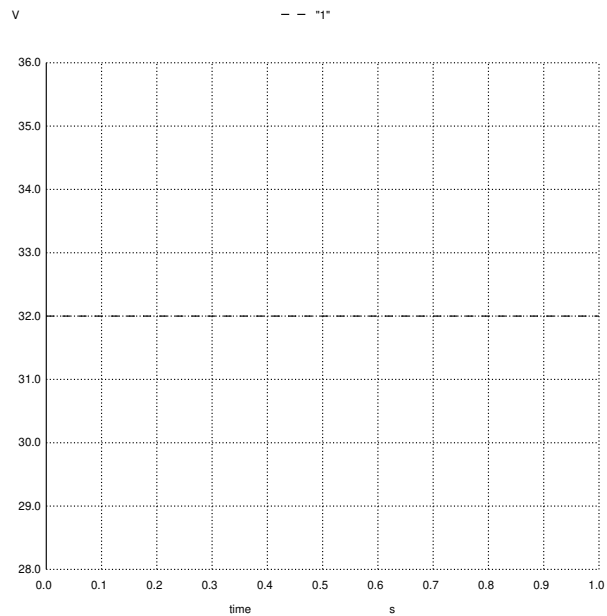

And here is the result of plot "2"

